



Sample Problems, Set 1

1. Minimal Two-Level Forms

Provide minimal sum-of-products and product-of-sums expressions for the following functions.

$$(a) f(a, b, c, d) = \bar{a}bc\bar{d} + \bar{a}bcd + abc\bar{d} + abcd + \bar{a}\bar{b}cd + \bar{a}b\bar{c}d + \bar{a}bc\bar{d} + \bar{a}bcd + abcd + ab\bar{c}d\bar{d}$$

$$(b) g(a, b, c, d) = \bar{a}bcd + \bar{a}\bar{b}cd + \bar{a}b\bar{c}d + \bar{a}bcd + \bar{a}bcd + \bar{a}bcd + \bar{a}\bar{b}cd + \bar{a}b\bar{c}d + \bar{a}bcd + abcd$$

$$(c) z(a, b, c, d, e, f) = abcdef + abcde\bar{f} + abcd\bar{e}\bar{f} + abcd\bar{e}f + ab\bar{c}d\bar{e}\bar{f} + ab\bar{c}d\bar{e}f + ab\bar{c}de\bar{f} + ab\bar{c}def + ab\bar{c}de\bar{f} + ab\bar{c}def + ab\bar{c}de\bar{f} + ab\bar{c}def + ab\bar{c}de\bar{f} + ab\bar{c}def + ab\bar{c}de\bar{f}$$

2. More Minimal Two-level Forms

Consider the example shown in Figure 1: a 7-segment display decoder. The inputs are four bits, x_0, x_1, x_2, x_3 , specifying a number in binary. The outputs are 7 bits, a, b, c, d, e, f, g , specifying which segments to light up in a display – such as that of a digital alarm clock – to form the image of the corresponding decimal number. Our goal is to design a circuit that implements the functions a, b, c, d, e, f, g (with 0 corresponding to “off” and 1 corresponding to “on”).

Since the four bits x_0, x_1, x_2, x_3 specify numbers from 0 to 15, but the display is only for 0 through 9, we’ll adopt the convention that for inputs corresponding to 10, 11, 12, 13, 14 and 15 *all* the segments should light up (i.e., a through g evaluate to 1 for these inputs).

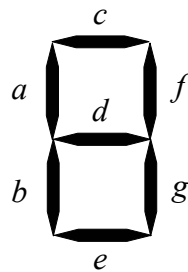


Figure 1: 7-Segment Display.

Fill in the following truth table.

| inputs | | | | outputs | | | | | | |
|--------|-------|-------|-------|---------|-----|-----|-----|-----|-----|-----|
| x_3 | x_2 | x_1 | x_0 | a | b | c | d | e | f | g |
| 0 | 0 | 0 | 0 | | | | | | | |
| 0 | 0 | 0 | 1 | | | | | | | |
| 0 | 0 | 1 | 0 | | | | | | | |
| 0 | 0 | 1 | 1 | | | | | | | |
| 0 | 1 | 0 | 0 | | | | | | | |
| 0 | 1 | 0 | 1 | | | | | | | |
| 0 | 1 | 1 | 0 | | | | | | | |
| 0 | 1 | 1 | 1 | | | | | | | |
| 1 | 0 | 0 | 0 | | | | | | | |
| 1 | 0 | 0 | 1 | | | | | | | |
| 1 | 0 | 1 | 0 | | | | | | | |
| 1 | 0 | 1 | 1 | | | | | | | |
| 1 | 1 | 0 | 0 | | | | | | | |
| 1 | 1 | 0 | 1 | | | | | | | |
| 1 | 1 | 1 | 0 | | | | | | | |
| 1 | 1 | 1 | 1 | | | | | | | |

Find minimal sum-of-product and product-of-sums expressions for a, b, c, d, e, f and g .

3. Timing Analysis

For the circuits in Figures 2, 3 and 4, compute the arrival times for each output function for each input combination.

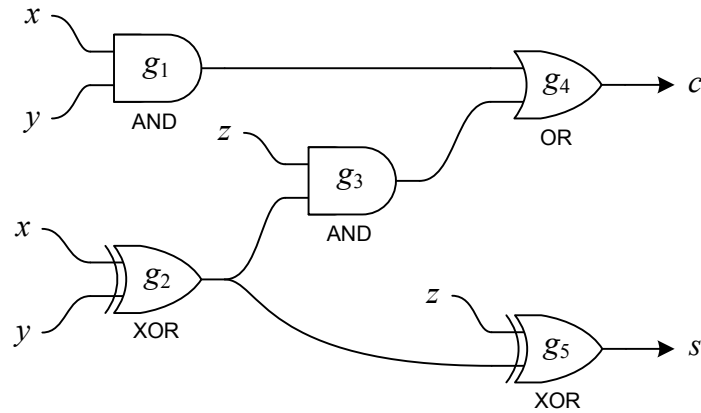


Figure 2: Circuit

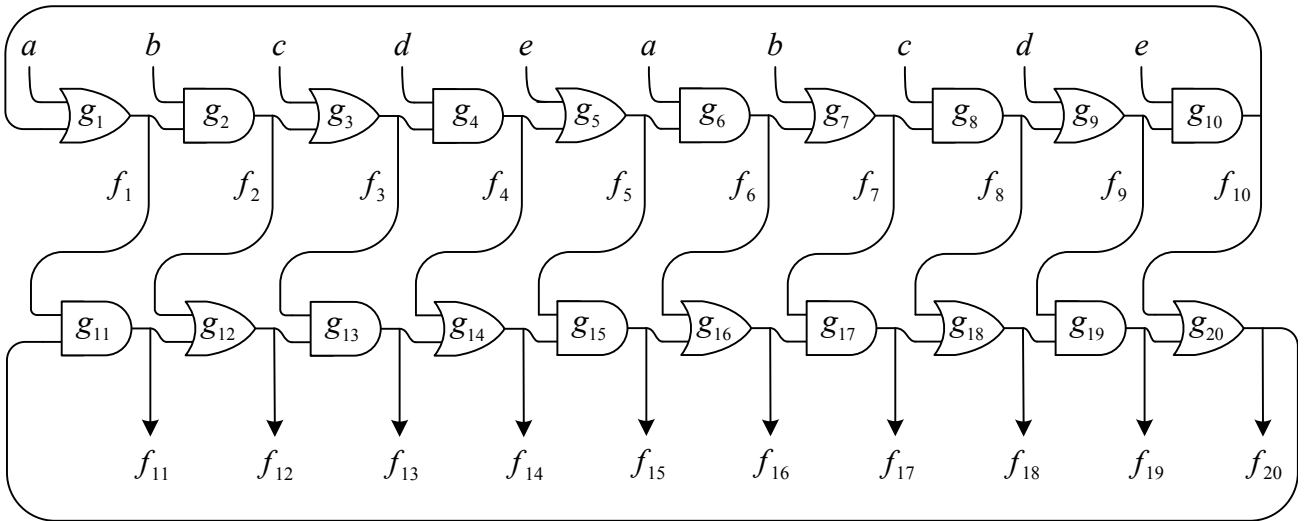


Figure 3: Circuit

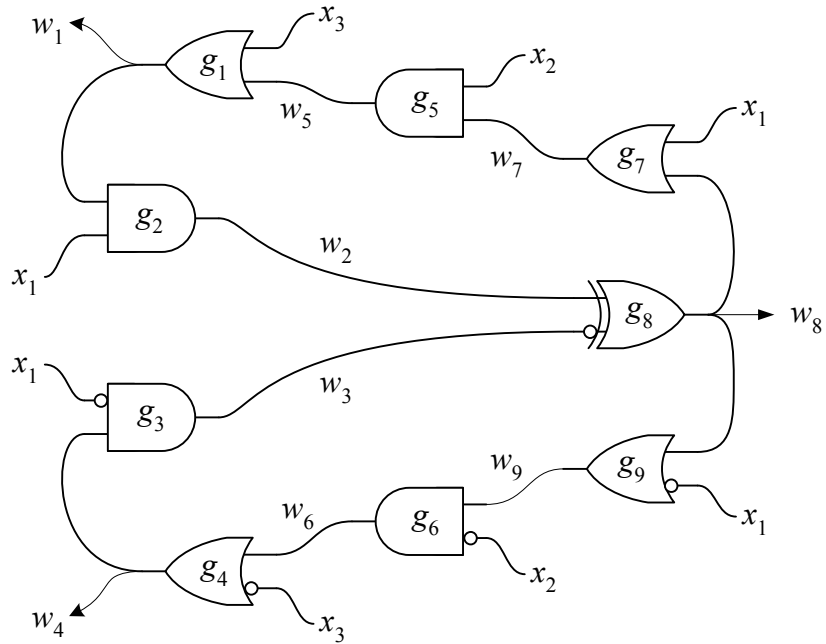


Figure 4: Circuit